
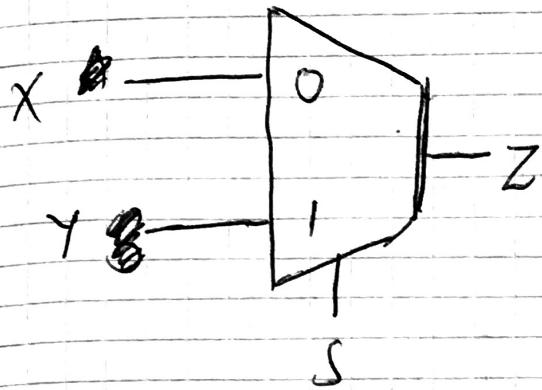



## 2 to 1 multiplexer

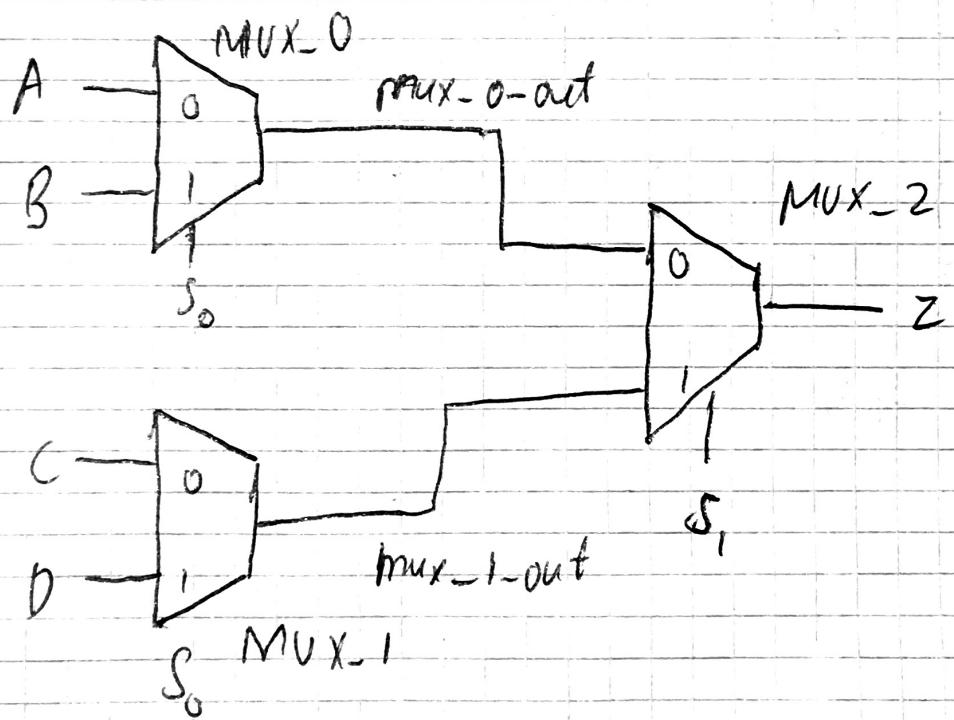



## 4 to 1 multiplexer



## 8 to 1 multiplexer

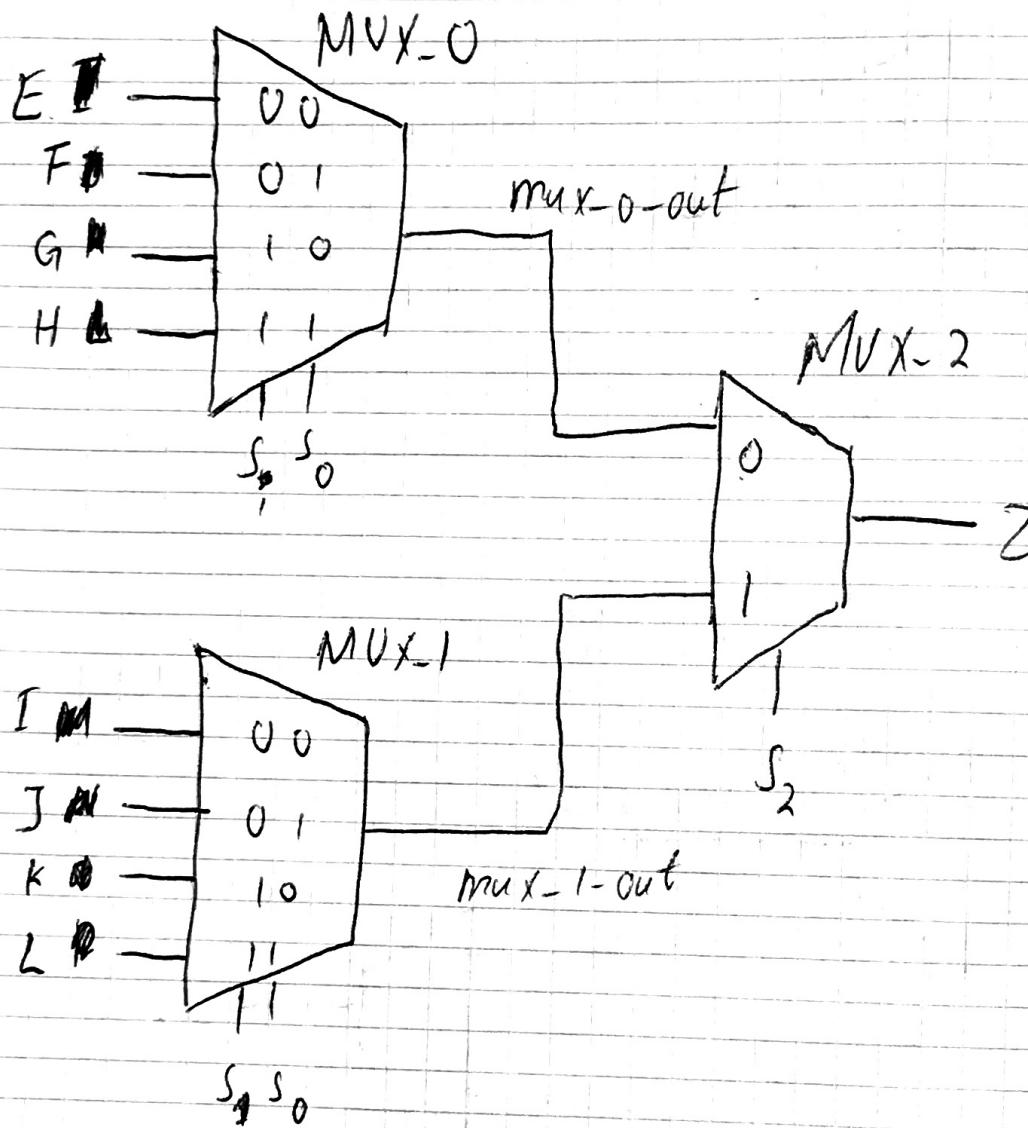


# 16 to 1 multiplexer

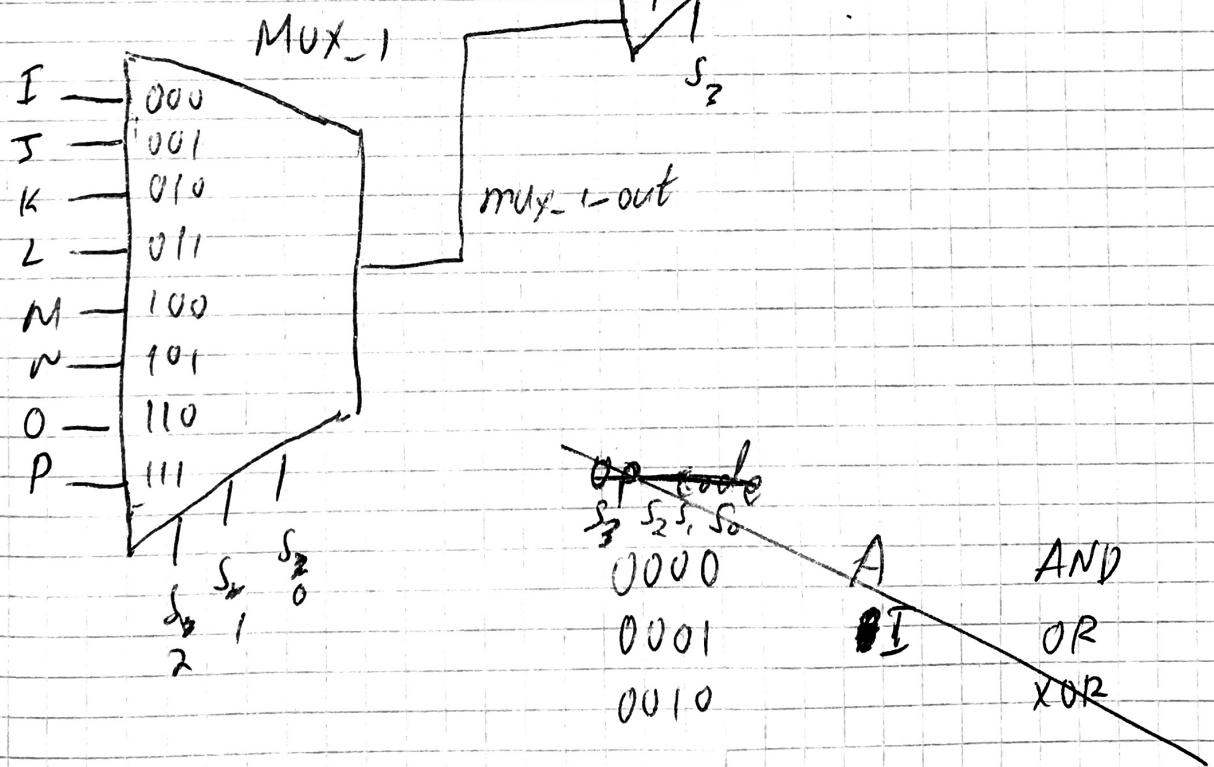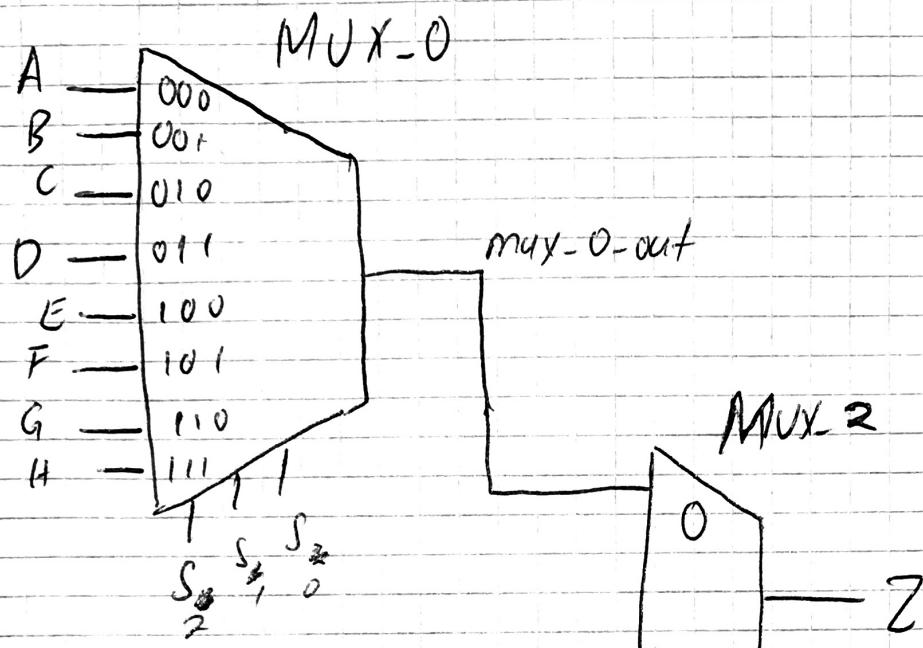

# Full Adder


Truth Table


Cin	A	B	Z	Cout
0	0	0	0	0
0	1	0	1	0
0	0	1	1	0
0	1	1	0	1
1	0	0	1	0
1	1	0	0	1
1	0	1	0	1
1	1	1	1	1

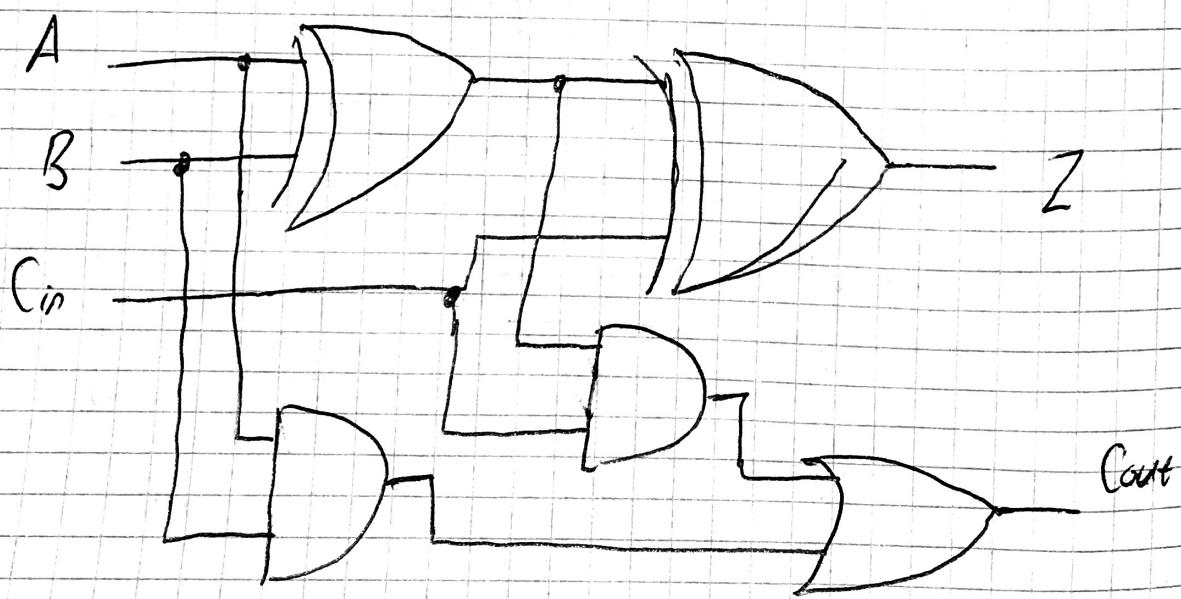

$$Z = (A \oplus B) \oplus C_{in}$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

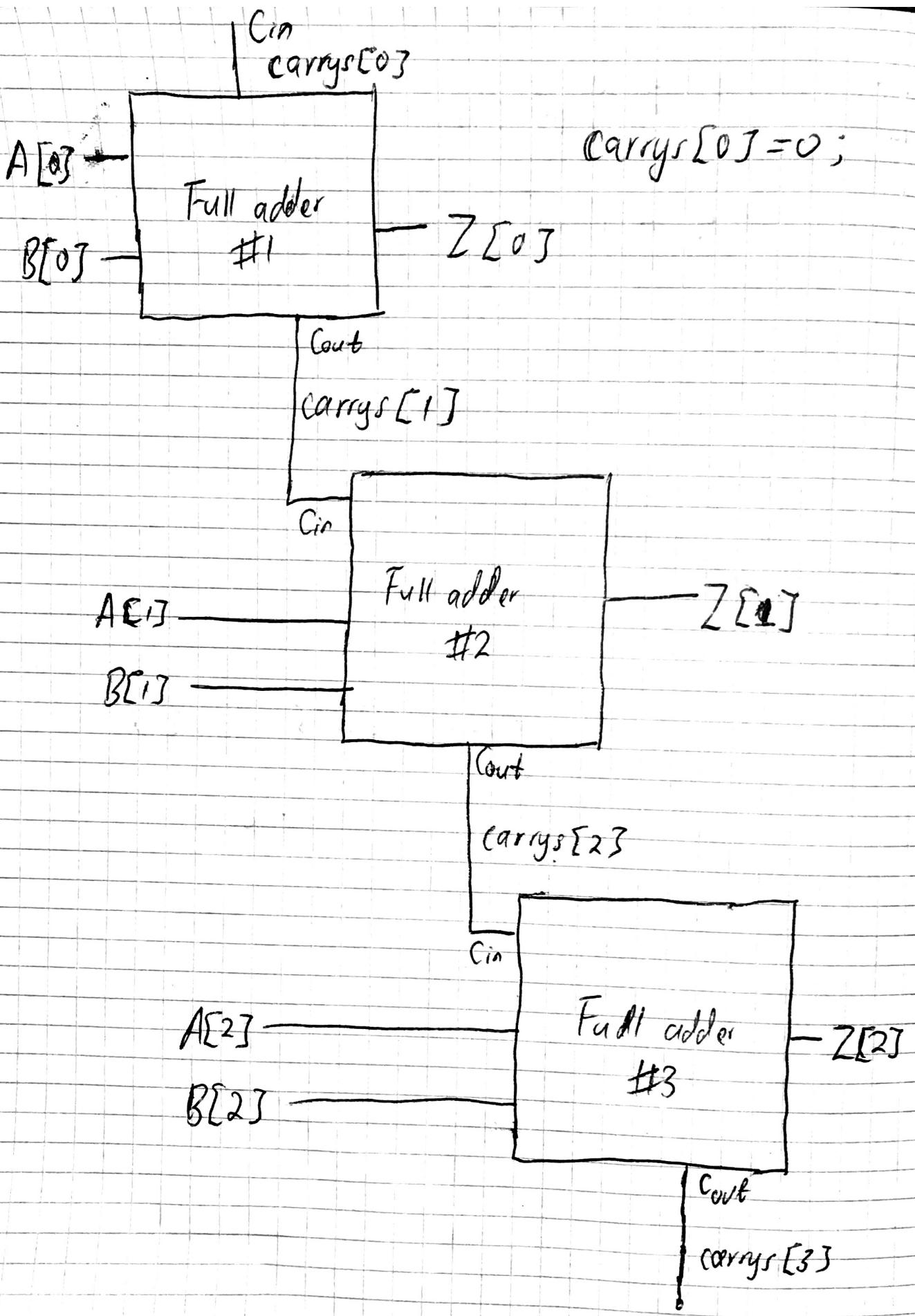

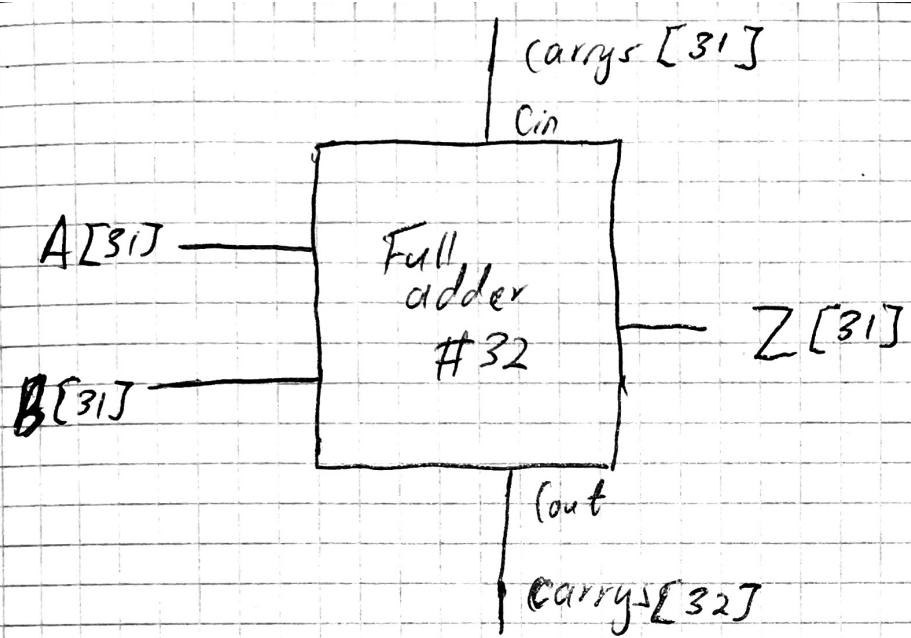

$$\text{overflow} = \text{carry}_{\{32\}}$$

SLT

$X$ MSB	$Y$ MSB	$X - Y$ MSB $c$	$z$ out
0	0	0	0
0	0	1	1
0	1	x	0
0	1	x	0
1	0	x	1
1	0	x	1
1	1	0	0
1	1	1	1

$X_{MSB}$  and  $Y_{MSB}$  indicate whether they are negative numbers  $\Rightarrow$  the only cases we need to care about are one both positive or both negative  $\Rightarrow$  look at the MSB of the calculation  $X - Y$ .

Using SOP on the MSBs

$$z = \cancel{\bar{x}\bar{y}c} + \bar{x}\bar{y} + XYZ$$

Equal

Wore 1s for equal bits and 0s for unequal bits

X	X	C
0	0	1
0	1	0
1	0	0
1	1	1

XNOR truth table

$$\Rightarrow X \text{XNOR } Y = 32^{\text{'}} b1$$

collapse to 1 if all bits are 1  $\Rightarrow$  AND the bits


$$\therefore \boxed{\text{AND}(X \text{XNOR } Y)}$$

Zero


If all output bits are zero, set. (i.e., don't set if only 1 bit is 1)

$$\boxed{\text{NOR}(\text{output})}$$


32 to 1 multiplexer

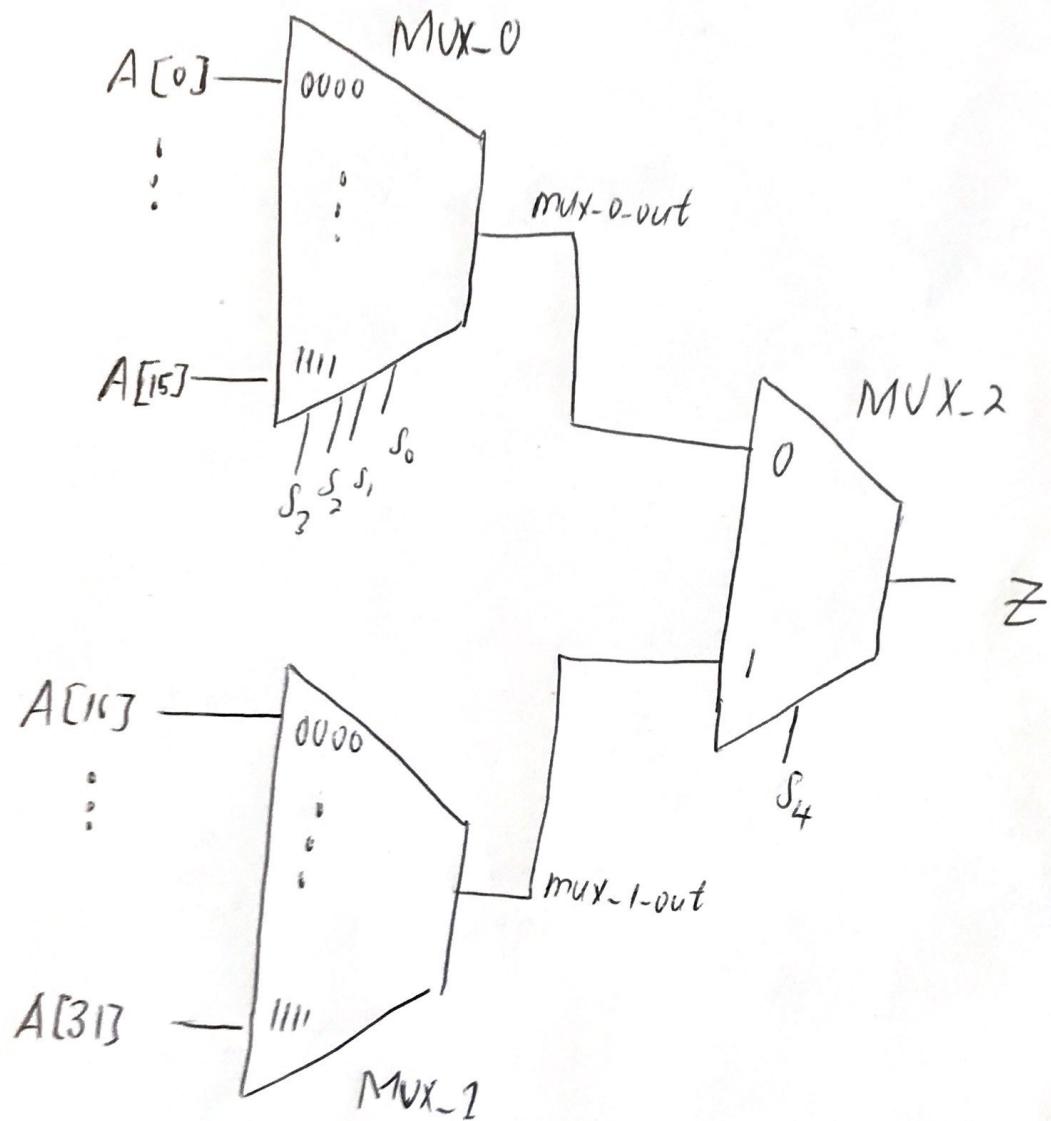



Subtractor.  $Z = A - B$

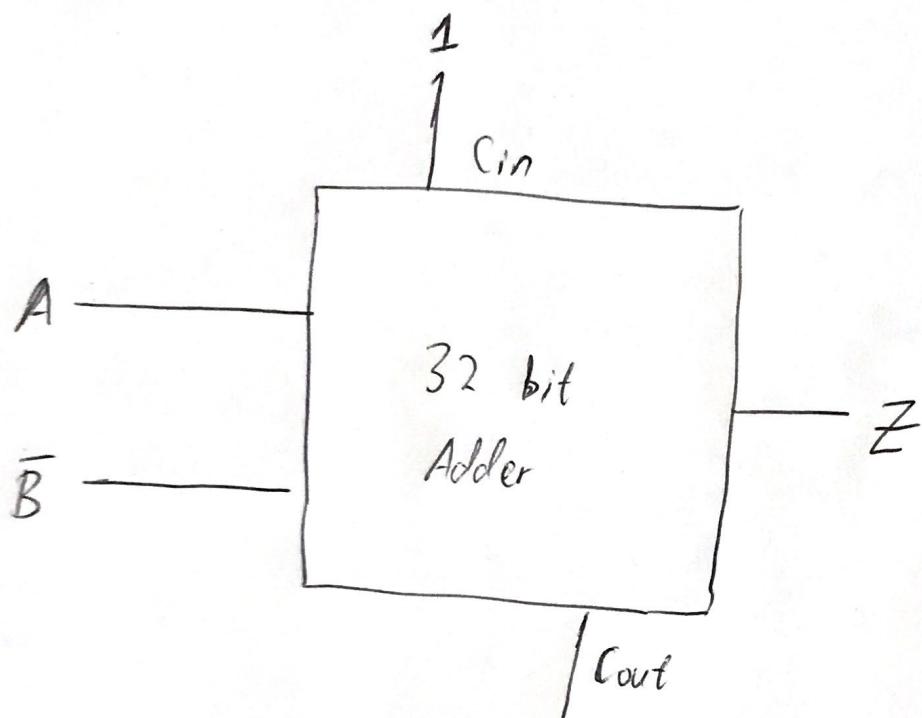

Shift left logical (SLL)

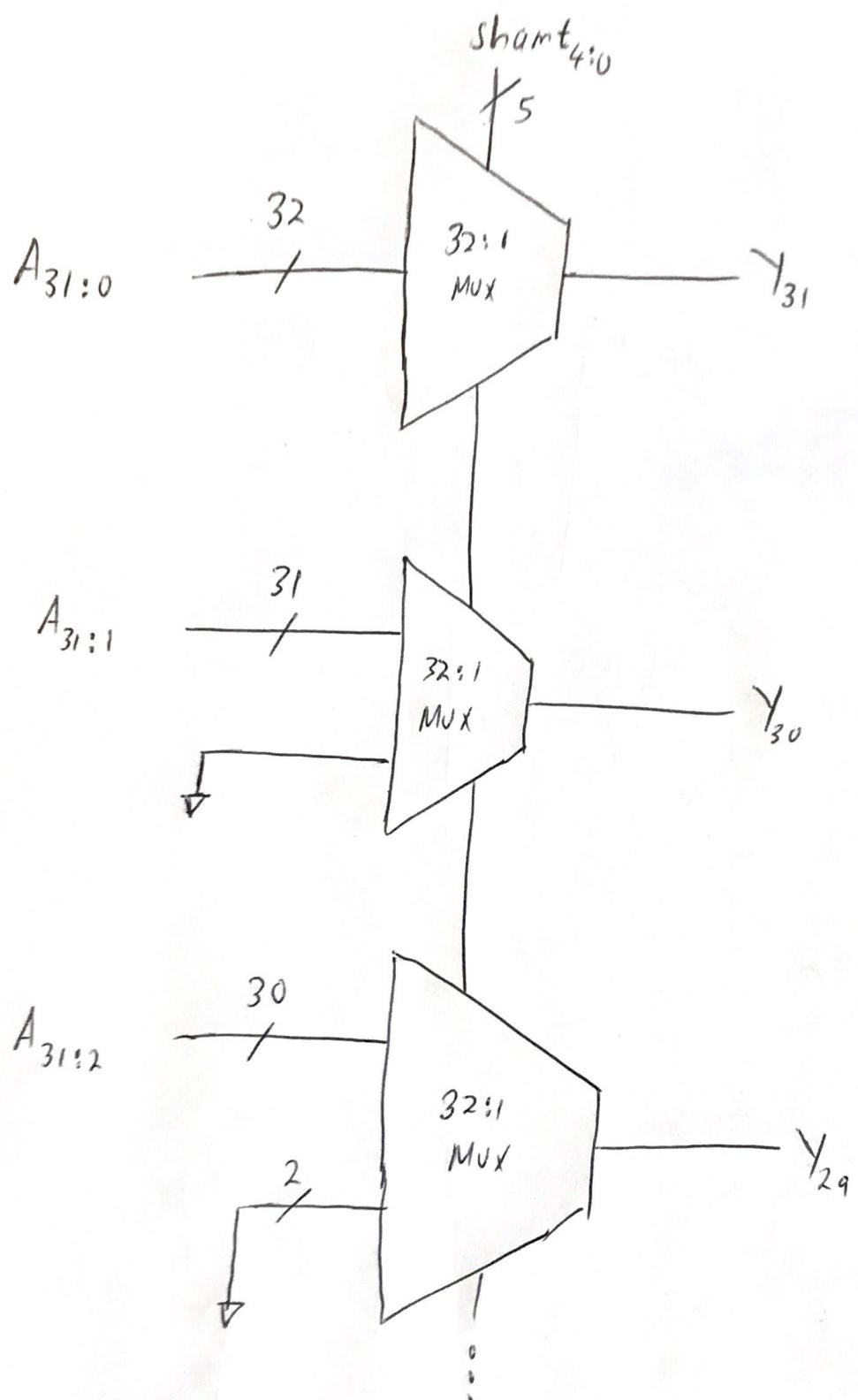

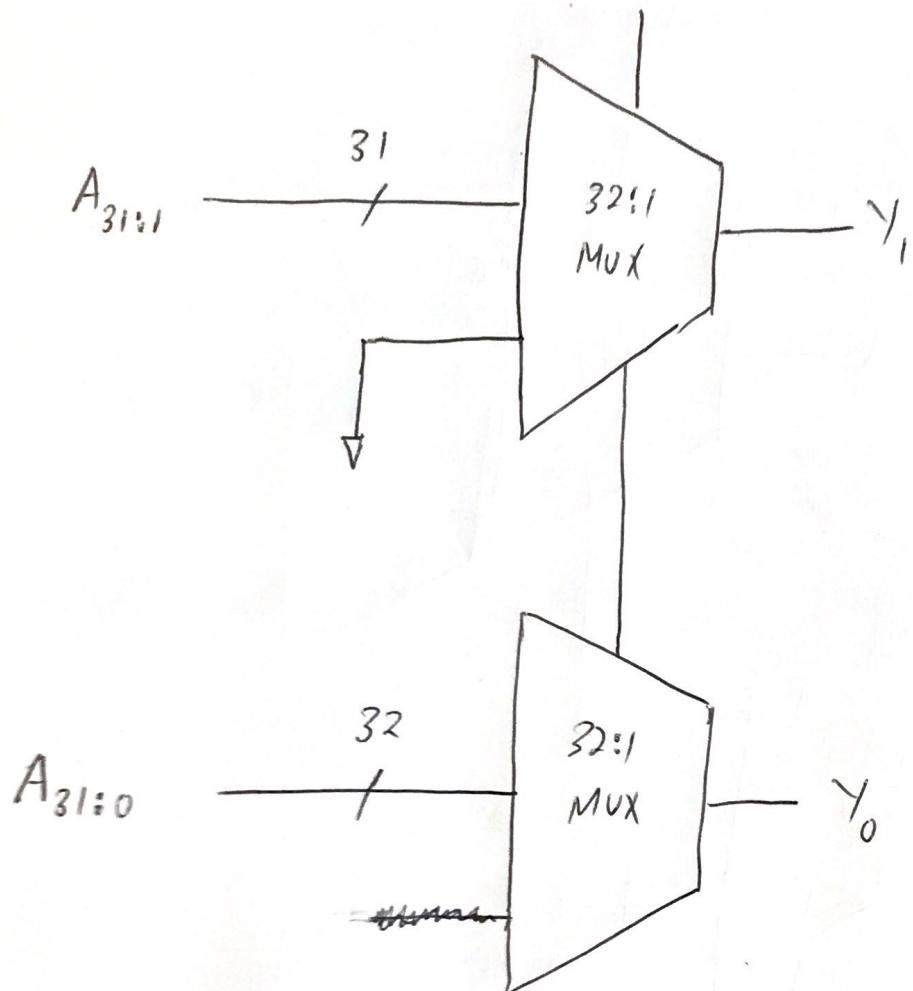

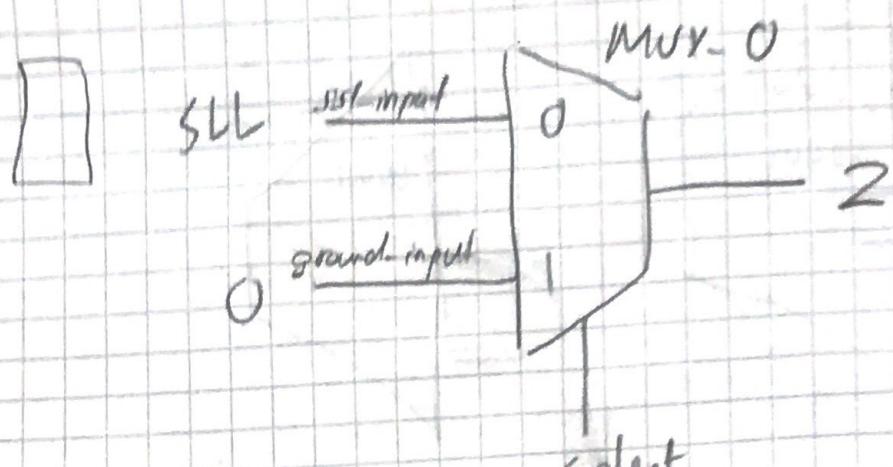

$$\text{Select} = OR(B(N-1:4))$$

Shift right logical (SRL)

